



Lab session #4

Activity #1: Majority-vote ALU


Design a hierarchical circuit consisting of 3 ALUs that perform the same operation, selected by the *ctrl* signal, on 3 distinct sets of 8-bit signals (*A* and *B* for ALU₀, *C* and *D* for ALU₁ and *E* and *F* for ALU₂). Use the ALU designed in activity #4 of Lab. 3. If:

- the 3 ALUs generate the same value, the circuit outputs that value on the 8-bit signal *decision* and the *data_valid* output is set to 1
- any 2 of the ALUs generate the same value, the circuit outputs that value on the 8-bit signal *decision* and the *data_valid* output is set to 1
- the 3 ALUs generate different values, the circuit outputs value *Z* on the 8-bit signal *decision* and the *data_valid* output is set to 0.

Create a suitable testbench with assertions to test the circuits on relevant values.

Activity #2: Reconfigurable ALU

Design a **reconfigurable ALU** composed of 4 4-bit ALUs processing two operands *A* and *B* whose size ranges from 4 to 16 bits. The operations are the same of the ALU designed in activity #4 of Lab. 3. An extra 4-bit input *nibble* selects the 4-bit group (a.k.a. nibble) that compose operands *A* and *B*. If the *i*-th bit in *nibble* is set to 1, the *i*-th group is part of the operand, as shown in the example of the following figure:

 

Modify the ALU designed in activity #4 of Lab. 3 so as to include an *enable* signal and to take into account carry-rippling between nibbles. When not enabled, each ALU outputs an all-0 result, carry-out included.

Create a testbench to simulate the circuit on relevant inputs. Use assertions.

Activity #3: Combinational adder-based multiplier

Designing a simple, though not optimal, combinational adder-based multiplier that resorts to the algorithm learned in elementary school.

The multiplication of two 4-bit numbers is illustrated in the following figure:

				a_3	a_2	a_1	a_0	multiplier
\times				b_3	b_2	b_1	b_0	
				a_3b_0	a_2b_0	a_1b_0	a_0b_0	
			a_3b_1	a_2b_1	a_1b_1	a_0b_1		
		a_3b_2	a_2b_2	a_1b_2	a_0b_2			
	a_3b_3	a_2b_3	a_1b_3	a_0b_3				
$+$								
	y_7	y_6	y_5	y_4	y_3	y_2	y_1	y_0
								product

The algorithm works in 3 steps:

- Multiply the digits of the multiplier (b_3 , b_2 , b_1 and b_0) by the multiplicand *A*. This corresponds to logically AND-ing b_i and the digits of *A*

