 


Lab session #10

Activity #1: Hardware FIFO


A queue is a component sometimes used during RTL design: it is written to at the back, it is read from the front. Writing is called an *enqueue*, reading is called a *dequeue*. As the first item written into a queue will be the first item read out, the queue is also called a *FIFO* (first-in-first-out):



Common use of queues includes:

- Computer keyboard: enqueues pressed keys onto queue, meanwhile dequeues and sends to computer
- Digital video recorder: enqueues captured frames, meanwhile dequeues frames, compresses them, and stores them
- Computer network routers: enqueue incoming packets onto queue, meanwhile dequeue packets, process destination information, and forward each packet out over appropriate port.

A queue is made of contiguous memory location, accessed by means of addresses and two pointers: *rear* and *front*, initially both pointing to 0. If the operation is an enqueue (write), the data is written to the address pointed to by *rear* and *rear* is incremented modulo the size of the queue. If the operation is a dequeue (read), the data is read from the address pointed to by *front*, *front* is incremented modulo the size of the queue.

 

Initially, then write A, followed by write B and by read

Two conditions are of interest:


- The queue is full: in an 8-entry queue, it means that 8 data are present and that no further enqueues are allowed until a dequeue occurs. The queue full condition causes $\text{front} = \text{rear}$
- The queue is empty: no dequeues are allowed until an enqueue occurs. The queue empty condition causes $\text{front} = \text{rear}$

As $\text{front} = \text{rear}$ in both cases, the solution adopted in hardware to detect whether $\text{front} = \text{rear}$ means full or empty resorts to a state machine that remembers if previous operation was enqueue or dequeue and accordingly sets full or empty output signal (respectively). Two flip-flops serve this purpose.

Design a 2^M -location FIFO for N-bit data as an FSM-D. Hint: according to the schematics in the following figure, use as **datapath** an $2^M \times N$ register file with 1 write and 1 read port to store data. Input *wr* starts a synchronous enqueue operation, provided the FIFO is not full. Input *rd* starts a synchronous dequeue operation, provided the FIFO is not empty. Enqueue and dequeue operations may occur at the same time. The output data from the FIFO is always available. Outputs *full* and



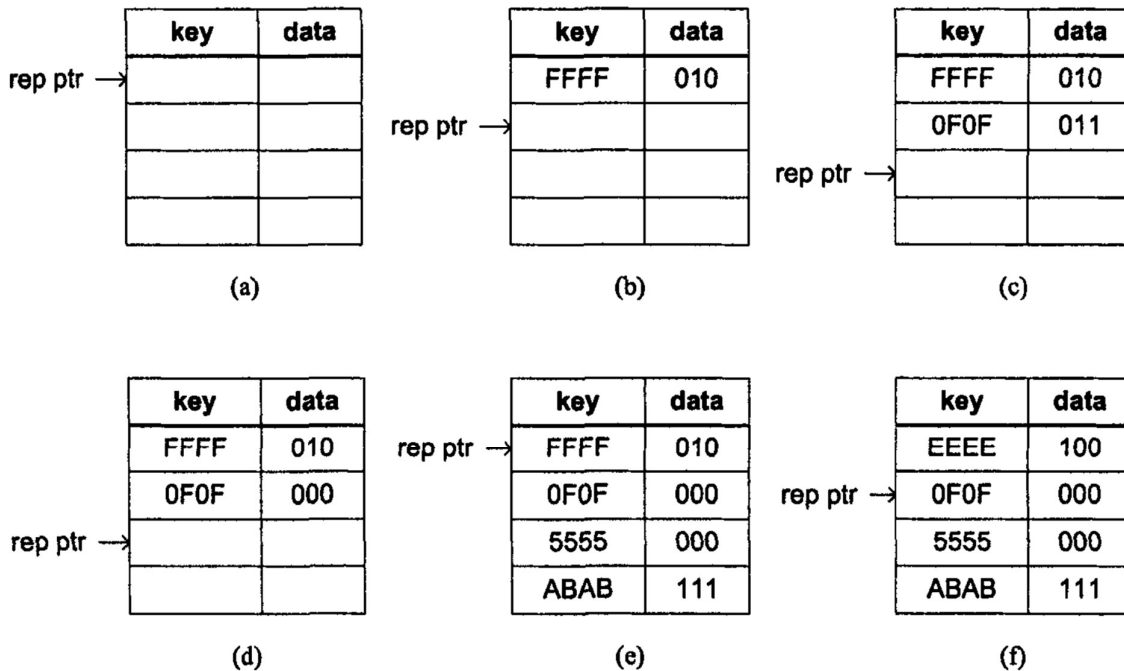- c) write (0F0F, 011): no match, write occurs at location pointed to by *rep_ptr*, which is then incremented
- d) write (0F0F, 000): match, replace 011 with 000, *rep_ptr* unchanged
- e) write (5555, 000) then (ABAB, 111): no match, 2 successive write operations occur at location pointed to by *rep_ptr*, which is incremented each time
- f) write (EEEE,100): no match, but CAM full, write occurs at location pointed to by *rep_ptr*. The content of the location pointed to by *rep_ptr* is discarded and overwritten with the new item.




Design a 4-word, 16-bit CAM as an FSM. Assumption: the stored key is unique, i.e. the number of matches is either 0 or 1. Hints: in the datapath separate the storage in 2: a register file for the data, accessed by means of its address and an array of 4 registers for the keys coupled with a matching circuit.


Signal *wr_en* selects whether is operation is write (*wr_en*=1) or read (*wr_en*=0).

Read: in the matching circuit, the output of each register of the key array is compared with the current value of the input key (i.e., the *key_in* signal) and a 1-bit matching signal (i.e., the *match(i)* signal) is generated accordingly. Since each stored key is unique, at most one can be matched. If for the *key_in* signal value there is a hit, a one bit *match* signal is asserted and a 2^2 -to-2 binary encoder generates the binary code of the matched location *addr*, output of the matching circuit. Signal *addr* in this case is routed on signal *addr_out*, connected to the read port address *r_addr* of the data file, and the corresponding data item is routed to the output. The output is not valid if the *hit* signal is not asserted. Register *rep_ptr* is updated.

In the following

 

 
represents a 16-bit register used to store the key. The following schematics shows the matching unit:



Write: given the key-data pair, if the key is a hit, the matching circuit will generate *addr_out*, connected to the write port address *w_addr* of the data file and the input data will be stored into the corresponding location. If the key is a miss, several tasks must be performed:

- Find an available register in the key array resorting to *rep_ptr*
- Store the input key into this register and update *rep_ptr*
- Store the data into the corresponding address in the data file.

 The following schematics represents the CAM:



Note that the schematics doesn't distinguish between control and status signals. Identify them , so as to comply with the FSM model that has a datapath and a controller.

Design three entities: *RegFileGen* for the register file containing the data, *KeyFile* for the key registers and the matching unit and *ReplPtr* for the register containing the replacement pointer and then interconnect them in a structural description of the datapath. The architectures of the 3 entities follow the behavioral description style. Design the controller and interconnect it in a structural description with the datapath to yield the CAM. Create a suitable testbench to test the CAM on relevant values.