



Lab session #02

October 4, 2024


Michelangelo Barocci, michelangelo.barocci@polito.it

PhD Student @ EDA Group - DAUIN

Politecnico di Torino


Before we start

❑ Vivado project structure:

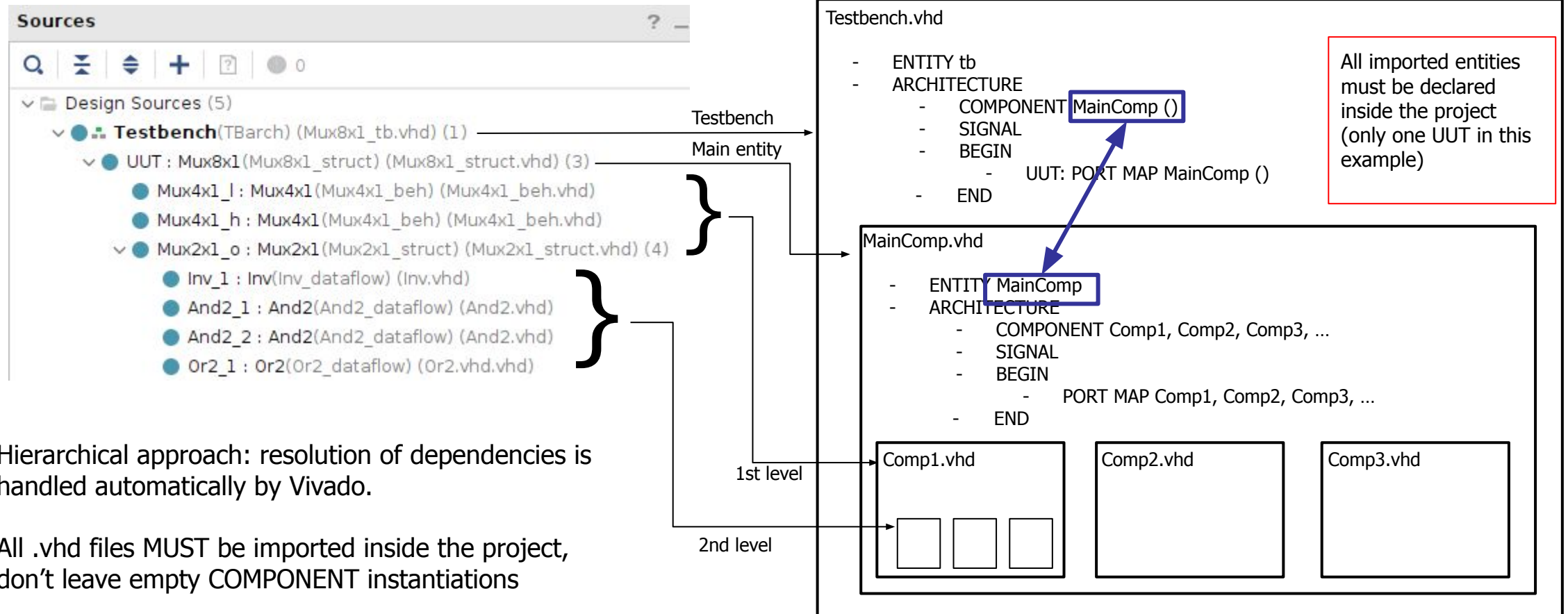


Before we start

- Vivado RTL structure:

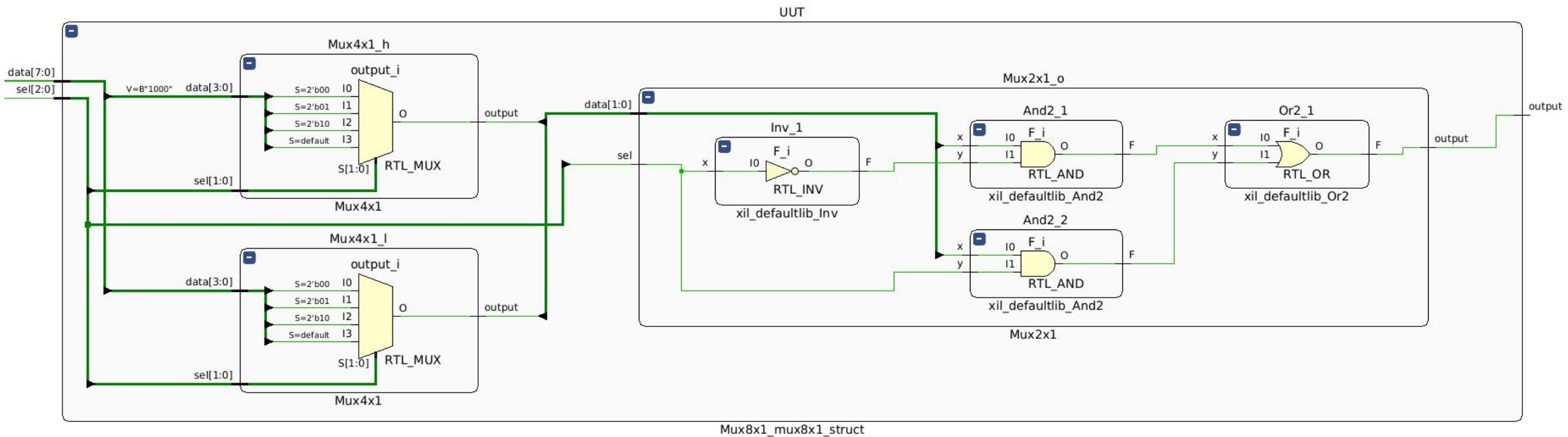


8to1 Multiplexer

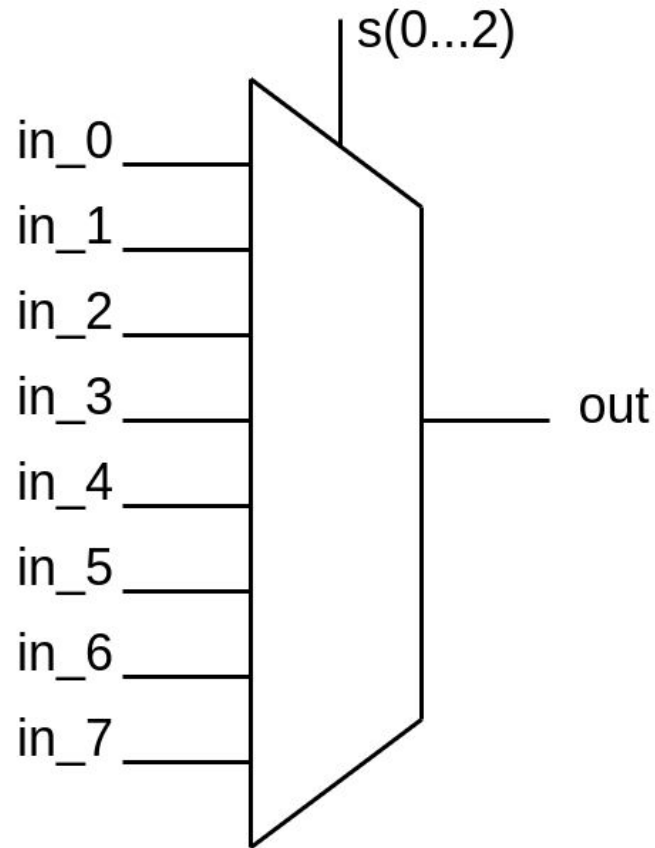

- ❑ Describe a 8to1 MUX using 5 different styles:
 - ❑ DATAFLOW with WHEN ELSE statements
 - ❑ DATAFLOW with WITH SELECT WHEN statement
 - ❑ BEHAVIORAL with IF THEN ELSIF statements
 - ❑ BEHAVIORAL with CASE WHEN statement
 - ❑ STRUCTURAL with a hierarchical approach (2x 4to1 BEHAVIORAL MUX and 1 2to1 STRUCTURAL MUX)
- ❑ Develop an appropriate testbench to perform the simulation and verify if the design is correct
- ❑ You should use a CONFIGURATION statement to enable switching between configurations


8to1 Multiplexer

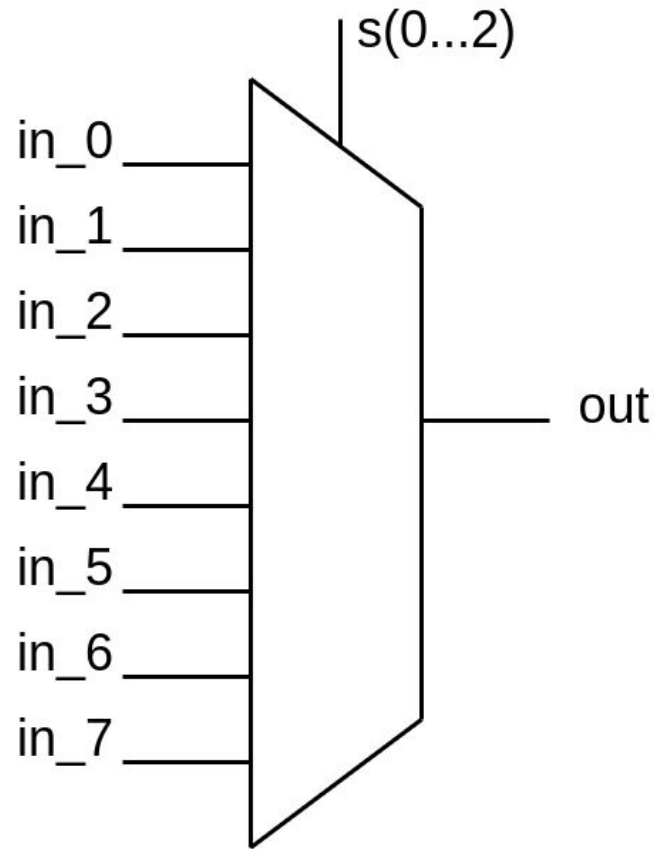

8to1 MUX truth table:


s0	s1	s2	out
0	0	0	in_0
0	0	1	in_1
0	1	0	in_2
0	1	1	in_3
1	0	0	in_4
1	0	1	in_5
1	1	0	in_6
1	1	1	in_7

3to8 Decoder

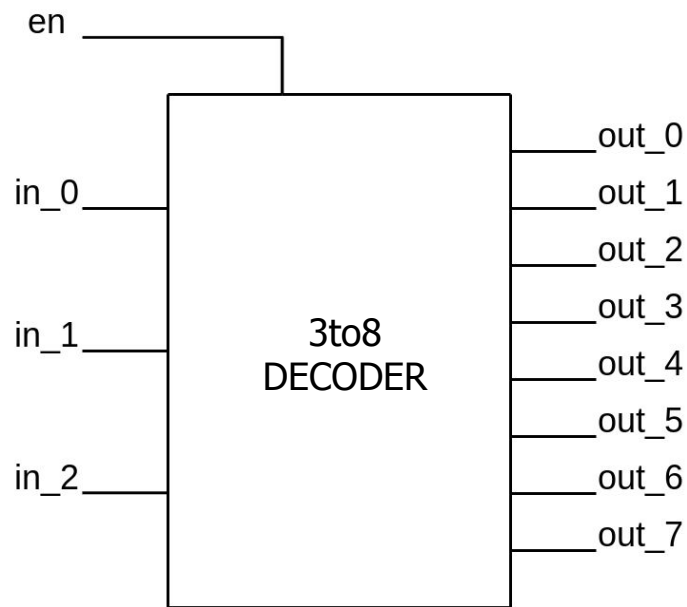

- ❑ Describe a 3to8 DECODER using 4 different styles:
 - ❑ DATAFLOW with WHEN ELSE statements
 - ❑ DATAFLOW with WITH SELECT WHEN statement
 - ❑ BEHAVIORAL with IF THEN ELSIF statements
 - ❑ BEHAVIORAL with CASE WHEN statement
- ❑ Develop an appropriate testbench to perform the simulation and verify if the design is correct


3to8 Decoder

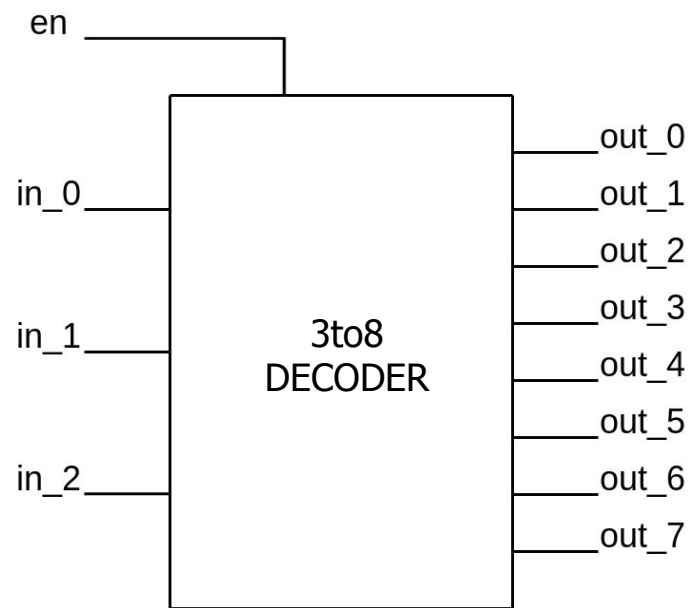

in_0	in_1	in_2	en	out_0	out_1	out_2	out_3	out_4	out_5	out_6	out_7
0	0	0	1	1	0	0	0	0	0	0	0
0	0	1	1	0	1	0	0	0	0	0	0
0	1	0	1	0	0	1	0	0	0	0	0
0	1	1	1	0	0	0	1	0	0	0	0
1	0	0	1	0	0	0	0	1	0	0	0
1	0	1	1	0	0	0	0	0	1	0	0
1	1	0	1	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	0	1
-	-	-	0	0	0	0	0	0	0	0	0





4to2 Priority Encoder

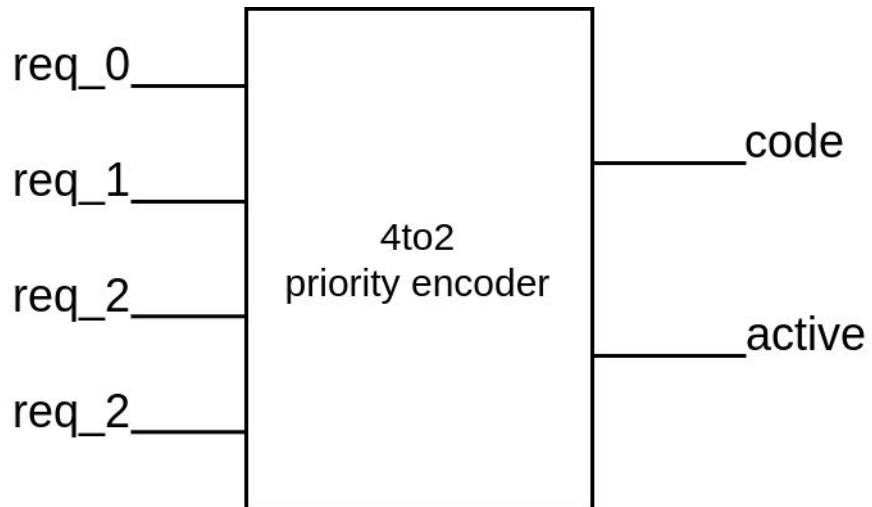

- ❑ Describe a 4to2 PRIORITY ENCODER using 4 different styles:
 - ❑ DATAFLOW with WHEN ELSE statements
 - ❑ DATAFLOW with WITH SELECT WHEN statement
 - ❑ BEHAVIORAL with IF THEN ELSIF statements
 - ❑ BEHAVIORAL with CASE WHEN statement
- ❑ Develop an appropriate testbench to perform the simulation and verify if the design is correct

4to2 Priority Encoder

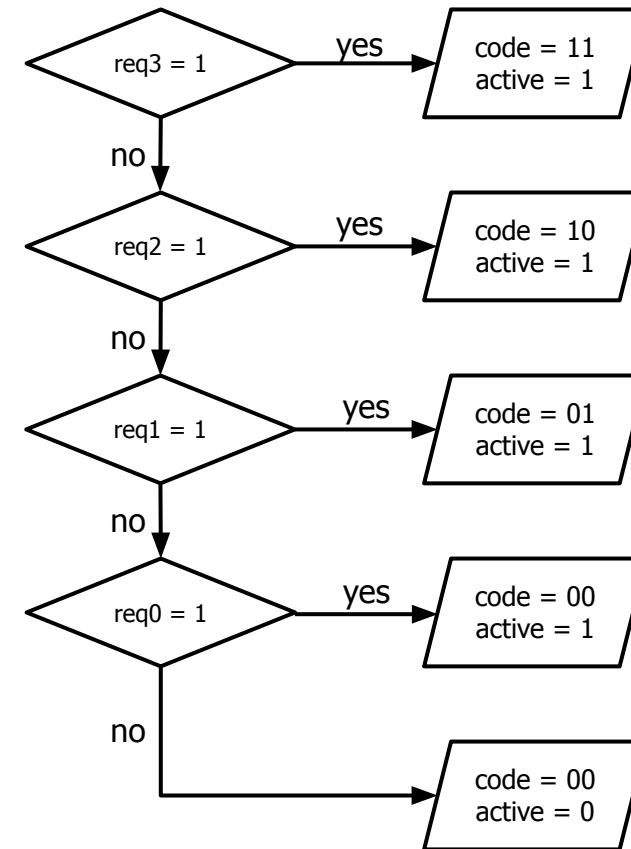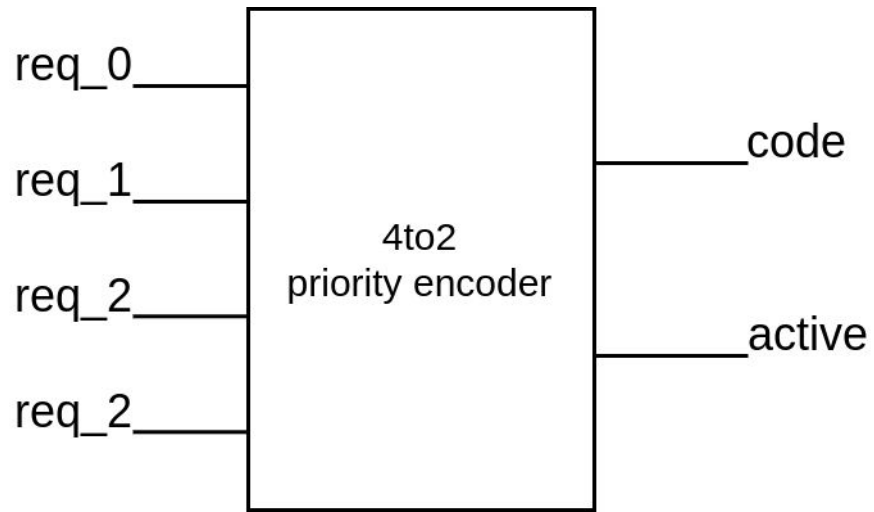



Synthesis

Lastly, run synthesis on your designed multiplexer, decoder and priority encoder.

- Understand the differences between the different description styles of the same circuit, do the reported results change?
- Are you able to estimate a maximum working frequency? How?