



Lab session #05

October 24, 2024


Michelangelo Barocci, michelangelo.barocci@polito.it

Politecnico di Torino,

PhD Student @ EDA Group - DAUIN


Dpt. of Computer and Control engineering (DAUIN)

FSM #1

 

- ❑ Design a Finite State Machine with these characteristics:
 - ❑ one input signal P to control the next state's decision
 - ❑ one output signal R (Moore output)
 - ❑ asynchronous reset
- ❑ Vary the design by:
 - ❑ Changing the type of state encoding (minimum length and one hot)
 - ❑ instantiating the FSM with 2 PROCESS and 1 PROCESS
- ❑ What changes?
- ❑ Write a testbench to test your FSM design on relevant inputs. Use a file to import input vectors and read expected output values.

FSM #2

 


- ❑ Design a Finite State Machine with these characteristics:
 - ❑ one input signal UpDw
 - ❑ one output signal (Mealy output)
 - ❑ asynchronous reset
- ❑ The state decision is made by reading the signal UpDw, that determines also the current state output. Follow the state diagram in the picture.
- ❑ To test the design use an external file to feed the input vectors to the testbench

Gray Counter

	b[3:0]	g[3:0]	
	0 0 0 0	0 0 0 0	
	0 0 0 1	0 0 0 1	
	0 0 1 0	0 0 1 1	
	0 0 1 1	0 0 1 0	
	0 1 0 0	0 1 1 0	
	0 1 0 1	0 1 1 1	
	0 1 1 0	0 1 0 1	
Binary Code →	0 1 1 1	0 1 0 0	← Gray Code
	1 0 0 0	1 1 0 0	
	1 0 0 1	1 1 0 1	
	1 0 1 0	1 1 1 1	
	1 0 1 1	1 1 1 0	
	1 1 0 0	1 0 1 0	
	1 1 0 1	1 0 1 1	
	1 1 1 0	1 0 0 1	
	1 1 1 1	1 0 0 0	

- ❑ Design an FSM-based N-bit Gray counter with asynchronous reset
- ❑ Remember how we implemented a Gray counter in Lab#03: now find a smart way to store the Current and Next state signals
- ❑ test your design with a testbench properly written for N=4

Decimal counter

 

- ❑ Design a BCD counter 0-999 by cascading three mod-10 (4-bit) counters: each counter represents a decade (100, 10 and 1) and has its own increment rules: a digit increments depending on the previous digit's current value
- ❑ Use a FSM-like approach: define the current and next digit of each counter as a finite state
- ❑ Test your design with a testbench and verify that all transitions are enabled correctly.